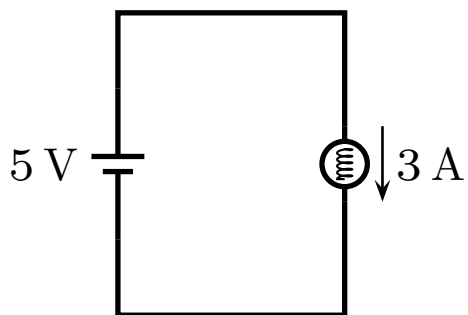


## Question 1

A bulb is connected to a battery as illustrated.




The current through the bulb and potential difference across the battery are indicated. The wires offer negligible resistance.

Which of the following is true?

1. In 10 s the total charge that flows through the bulb is 3 C and through the battery 3 C.
2. In 10 s the total charge that flows through the bulb is 5 C and through the battery 5 C.
3. In 10 s the total charge that flows through the bulb is 30 C and through the battery 5 C.
4. In 10 s the total charge that flows through the bulb is 30 C and through the battery 30 C.
5. In 10 s the total charge that flows through the bulb is 30 C and through the battery 50 C.
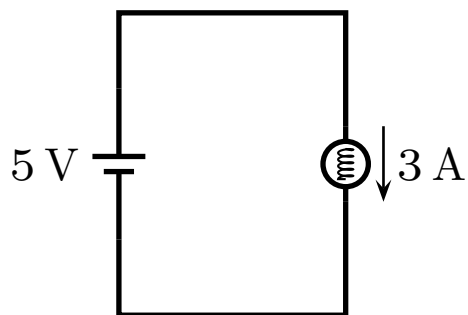
## Question 2

A bulb is connected to a battery as illustrated.




The current and potential difference across the battery are indicated. The wires offer negligible resistance.

In  $2\text{ s}$  a total of  $6\text{ C}$  moves from the positive to negative terminal of the battery. Which of the following is true?

1. The energy lost by this charge is  $0\text{ J}$ .
2. The energy lost by this charge is  $3\text{ J}$ .
3. The energy lost by this charge is  $5\text{ J}$ .
4. The energy lost by this charge is  $6\text{ J}$ .
5. The energy lost by this charge is  $30\text{ J}$ .
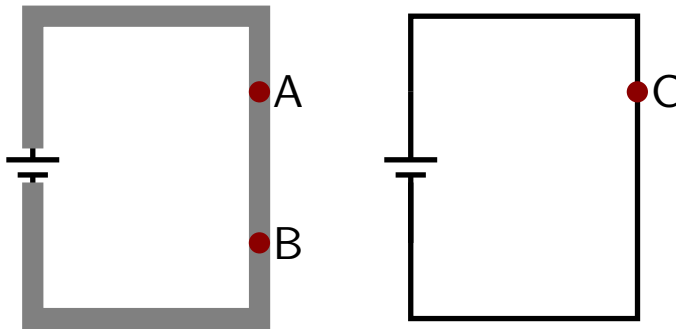
## Question 3

Two identical batteries are connected in two different scenarios as illustrated. In the scenario on the left a thicker wires (smaller resistance) are used.




Which of the following represents the rank of the magnitude of the currents?

1.  $I_A = I_B = I_C$
2.  $I_A = I_B > I_C$
3.  $I_C > I_A = I_B$
4.  $I_B > I_A = I_C$
5.  $I_C = I_A > I_B$

## Question 4

Consider the following circuit.

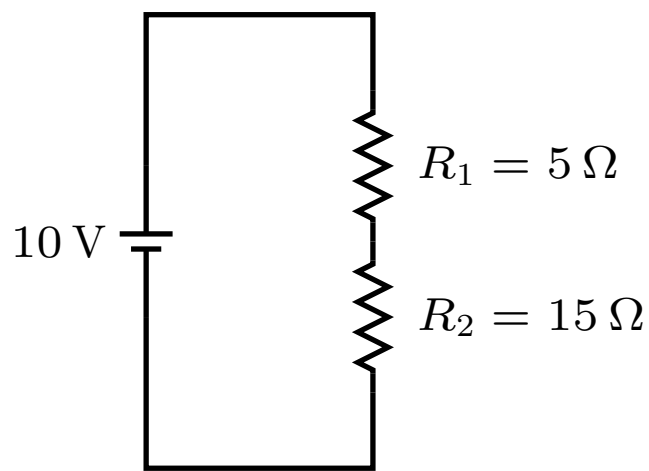

Which of the following best represents the potential difference across each of the resistors?

1.  $\Delta V_1 = \frac{1}{3} \Delta V_2$
2.  $\Delta V_1 = \frac{1}{2} \Delta V_2$
3.  $\Delta V_1 = \Delta V_2$
4.  $\Delta V_1 = 3\Delta V_2$
5. Not enough info/none of the above.