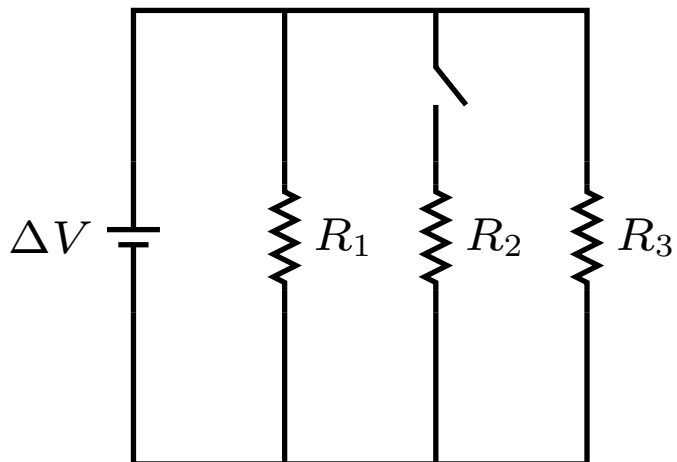


Question 1

Consider the following circuit, where $R_1 = R_2 = R_3$.




Consider the current through resistor 3 when the switch is open versus when it is closed.

1. $I_{\text{closed}} = \frac{2}{3} I_{\text{open}}$
2. $I_{\text{closed}} = I_{\text{open}}$
3. $I_{\text{closed}} = \frac{3}{2} I_{\text{open}}$

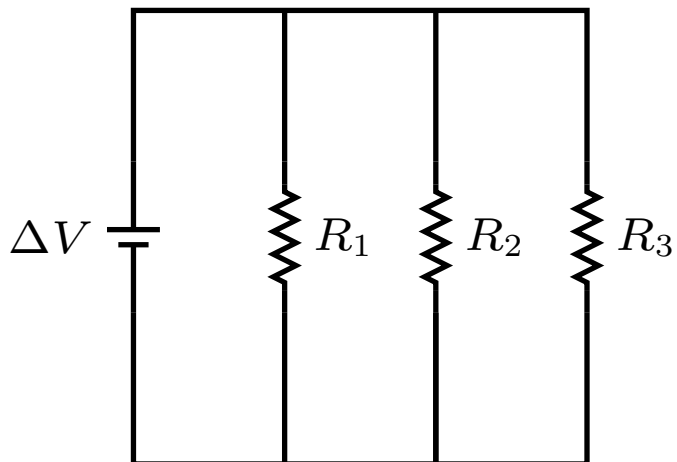Question 2

Consider the following circuit, where $R_1 = R_2 = 10\ \Omega$, $R_3 = 20\ \Omega$.




Which of the following is true of the equivalent resistance of the entire combination?

1. $R_{\text{eq}} = 40\ \Omega$
2. $20\ \Omega \leq R_{\text{eq}} < 40\ \Omega$
3. $10\ \Omega \leq R_{\text{eq}} < 20\ \Omega$
4. $R_{\text{eq}} = 10\ \Omega$
5. $R_{\text{eq}} < 10\ \Omega$

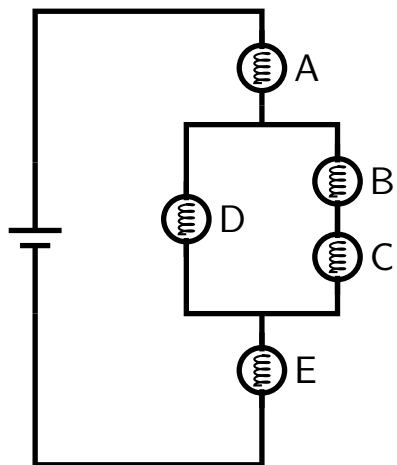Question 3

Several identical bulbs are connected in a circuit as illustrated.



Assume that the bulbs obey Ohm's law.

Which of the following statements about the powers produced by bulbs B versus D are true (choose one)?

1. $P_D = 4P_B$
2. $P_D = 2P_B$
3. $P_D = P_B$
4. $P_D = \frac{1}{2} P_B$
5. $P_D = \frac{1}{4} P_B$