

Weds: Discussion / quiz


Ex 82, 83, 84, 85, 86, 87, 92, 93

Thurs: Warm Up 6 D2LCircuit Operation

A circuit operates by having a current of charged particles flow through various circuit elements. The following quantities are useful for understanding circuits:


- 1) current ~ rate at which charge flows past any point

$$I = \left| \frac{\Delta Q}{\Delta t} \right| \quad \text{Amps}$$

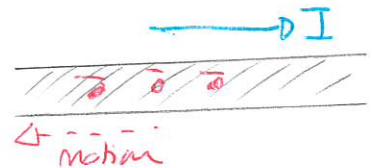

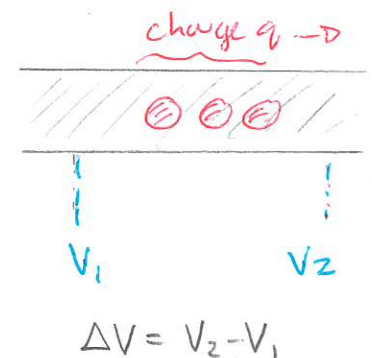- 2) potential difference ~ energy (per unit charge) to transport charge from one location to another.


$$\begin{aligned} &\text{Energy to move charge } q \\ &= q \Delta V \end{aligned} \quad \text{Volts}$$



These have analogs with flow of water around pipes:

current ~ rate at which volume passes

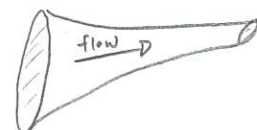potential difference ~ pressure difference between ends



Quiz 1 80% - 100%

Quiz 2 30% - 70%


Ohm's Law

We are typically well-equipped with batteries and other power supplies that can produce a known potential difference. The question will then be what current results when this is connected to any particular device.

Demo: PhET circuit AC

* connect for different bulbs

* observe V and I using meters

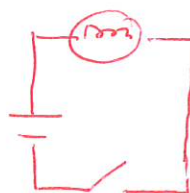


The exact relationship between the potential difference across a device and the current depends on the type of device. An experimental observation applies to a large class of devices; called Ohmic devices.

The potential difference across an Ohmic device, ΔV , and the current through the device, I , are related via:

$$\Delta V = IR$$

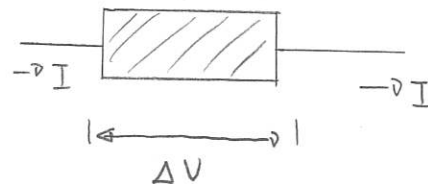where R is a constant for the particular device called the resistance of the device.




This is called Ohm's Law. The units of resistance are: $\text{Ohms} \equiv \Omega = \frac{V}{A}$

Examples include *wires
*resistors

The resistance of a device depends on:

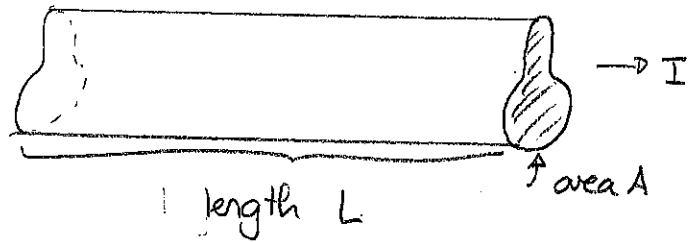- 1) its configuration
- 2) the material from which it is constructed

A general rule applies for an Ohmic object with a cylindrical cross section. For current that flows perpendicular to the cross-section; the resistance is:



$$R = \rho \frac{L}{A}$$

where L = length of material

A = cross sectional area

ρ = resistivity of the material.

"rho"

The resistivity primarily depends on the type of material and to a lesser degree on the temperature.


Quiz 3 - not done

Basic circuit laws

We can now develop quantitative laws that apply to any circuit.

First the conservation of charge implies

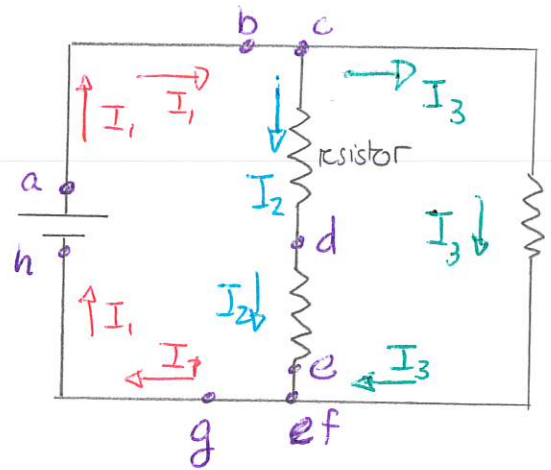- 1) in any single arm of a circuit the current is the same
- 2) at any junction the current leaving equals the current entering.
In the example $I_1 = I_2 + I_3$



Second the conservation of energy implies

- 3) the potential differences around any single closed loop must add to zero. (Kirchoff's loop rule)

In the example, letting $\Delta V_{a \rightarrow b} = V_b - V_a$ we get

$$\Delta V_{a \rightarrow b} + \Delta V_{b \rightarrow c} + \Delta V_{c \rightarrow d} + \Delta V_{d \rightarrow e} + \Delta V_{e \rightarrow f} + \Delta V_{f \rightarrow g} + \Delta V_{g \rightarrow h} + \Delta V_{h \rightarrow a} = 0$$

Then across any section of wire $\Delta V = 0$. Thus

$$0 + 0 + \Delta V_{c \rightarrow d} + \Delta V_{d \rightarrow e} + \Delta V_{h \rightarrow a} = 0$$

$$\Rightarrow \underbrace{-\Delta V_{h \rightarrow a}}_{= -\Delta V_{a \rightarrow h}} = \Delta V_{c \rightarrow d} + \Delta V_{d \rightarrow e}$$

$$\Rightarrow \underbrace{\Delta V_{a \rightarrow h}}_{\text{battery}} = \underbrace{\Delta V_{c \rightarrow d}}_{\text{resistor 1}} + \underbrace{\Delta V_{d \rightarrow e}}_{\text{resistor 2}}$$

Power in Circuits

An important issue with circuit elements is the rate at which they consume or deliver energy. This is quantified by power:

Power ~ rate at which energy is consumed / delivered

If energy ΔE is consumed / delivered in time Δt then the power is

$$P = \frac{\Delta E}{\Delta t}$$


units: Watts $\hat{=}$ $W = \frac{J}{s}$

This is easy to measure and compute in electric circuit elements.

The energy required is

$$\begin{aligned}\Delta E &= \Delta U_{elec} \\ &= (\Delta Q) \Delta V\end{aligned}$$
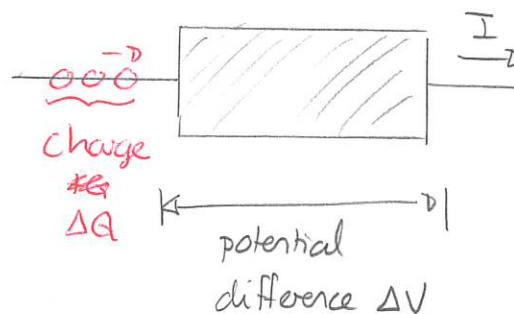
$$\Rightarrow P = \underbrace{\frac{\Delta Q}{\Delta t}}_I \Delta V$$



Thus

If current I flows through a device across which the potential difference is ΔV then

$$P = I \Delta V$$

For Ohmic devices

$$\Delta V = IR \quad \text{or} \quad I = \frac{\Delta V}{R}$$

$$P = I(IR)$$

$$P = I^2 R$$

$$P = \frac{\Delta V}{R} \Delta V$$

$$P = \frac{\Delta V^2}{R}$$