

* Thurs: Exam II in class

Covers: Ch 26.5 $\rightarrow$ 26.6

Ch 27.

Ch 28

Lectures 12-19

HW 5,6

Bring: * Calculator

* Previous 3" x 5" single side card

* Second 3" x 5" single side card.

Study * 2017 Exam II Q1 $\rightarrow$ 4

* 2018 Exam II Q1-9

* HW, Discussion Probs, Discussion Quizzes

* Class quizzes

Chapter 25.5 - 26.6 (Capacitors)

$$Q = C \Delta V_c \quad C = \frac{\epsilon_0 A}{d} \text{ (Parallel Plate)}$$

$$U_c = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} C (\Delta V_c)^2$$

$$C_{eq} = C_1 + C_2 \text{ (parallel)}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \text{ (series)}$$

Quiz 1 80%

Additional Circuits Problems

125 Capacitors in Series: Energy

Two capacitors are connected in series. Determine an expression for ~~or~~ the energy stored in each capacitor, *for the*

case where $C_2 = 2C_1$

Answer: The charge on each capacitor is the same. So for capacitor 1

$$U_1 = \frac{1}{2} \frac{Q^2}{C_1}$$

For capacitor 2

$$U_2 = \frac{1}{2} \frac{Q^2}{C_2}$$

We just need the charge. This comes from

$$Q = C_{eq} \Delta V$$

and


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_1} + \frac{1}{2C_1} = \frac{2+1}{2C_1} \Rightarrow C_{eq} = \frac{2}{3} C_1$$

$$Q = \frac{2}{3} C_1 \Delta V$$

Then

$$U_1 = \frac{1}{2} \left(\frac{2}{3} C_1 \Delta V \right)^2 \frac{1}{C_1} = \frac{1}{2} \frac{4}{9} \frac{C_1^2 \Delta V^2}{C_1} = \frac{2}{9} \frac{\Delta V^2}{C_1}$$

$$U_2 = \frac{1}{2} \left(\frac{2}{3} C_1 \Delta V \right)^2 \frac{1}{C_2} = \frac{1}{2} \frac{4}{9} \frac{C_1^2 \Delta V^2}{2C_1} = \frac{1}{9} \frac{\Delta V^2}{C_1}$$

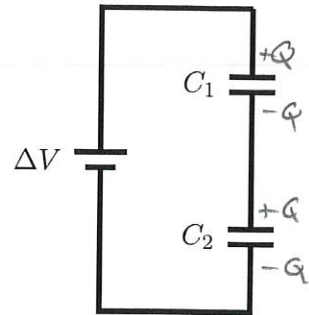

Chapter 27

$$J = \frac{\Delta Q}{\Delta t}$$

$$R = \frac{\rho L}{A}$$

$$I = \frac{\Delta V}{R}$$

$$\Delta V = IR$$

$$P = I \Delta V$$

Example: Quiz 2 70% ~ 100%

126 Electrons in a circuit

A 220Ω resistor is connected to a 9.0 V battery.

- a) Determine the number of electrons that flow past any point in the circuit in 30 s .
- b) Determine the amount of energy needed to push a single electron through the resistor.

Answer: a) $I = \frac{\Delta Q}{\Delta t}$ would give $\Delta Q = I \Delta t$

Then let N be the number of electrons

$$\Delta Q = Ne \Rightarrow N = \frac{\Delta Q}{e}$$

Now $I = \frac{\Delta V}{R} = \frac{9.0\text{ V}}{220\Omega} = 0.041\text{ A}$

$$\Delta Q = 0.041\text{ A} \times 30\text{ s} = 1.2\text{ C}$$

$$N = \frac{1.2\text{ C}}{1.6 \times 10^{-19}\text{ C}} = 7.7 \times 10^{18} \text{ electrons}$$

b) $\Delta U = q \Delta V \Rightarrow \Delta U = e \Delta V$

$$= 1.6 \times 10^{-19}\text{ C} \times 9.0\text{ V}$$

$$\Delta U = 1.4 \times 10^{-18}\text{ J}$$

Chapter 28

$$P = I \Delta V$$

$$\Delta V = I R_{eq}$$

series: $R_{eq} = R_1 + R_2 + R_3 + R_4 \dots + R_N$


parallel: $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$

Example: Quiz 3 ~ 40% ~ 90%


127 Resistors in series and parallel, 2

- a) Determine the currents through and voltages across each resistor in the illustrated circuit.
- b) Determine the potential difference between points A and B.

(132S22)

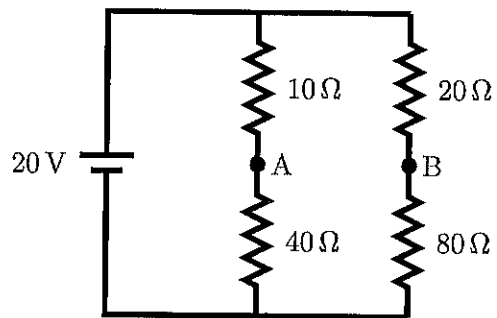

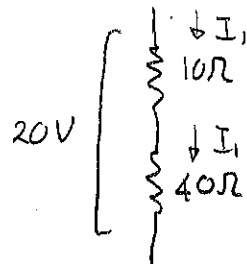Answer: a) The potential difference across each arm is 20V



$$\Delta V = I_1 R_{eq}$$

$$R_{eq} = 10\Omega + 40\Omega = 50\Omega$$


$$20V = I_1 50\Omega$$

$$\Rightarrow I_1 = 0.40A$$

This is the current in the 10Ω and 40Ω resistors. Then for each

$$\Delta V = I_1 R \Rightarrow \Delta V = 0.40A R$$

Then for the other arm

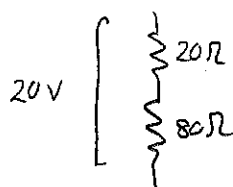

$$\Delta V = I_2 R_{eq}$$

$$R_{eq} = 20\Omega + 80\Omega = 100\Omega$$

$$20V = I_2 100\Omega \Rightarrow I_2 = 0.20A$$

Resistor	I	ΔV
10Ω	0.40A	4.0V
40Ω	0.40A	16V
20Ω	0.20A	4.0V
80Ω	0.20A	16V

We get the individual voltages via $\Delta V = IR = 0.20AR$.

- b) The potential at A is the same as B. So potential difference between these is 0V